
ELEC 4700 Assignment 4

Table of Contents

Circuit Modeling	1
Section 1: Revisiting PA7 and Assignment 3	1
Section 1.1: Finding the Resistance of R3	1
Section 1.2: Calculating the resistance of R3	11
Section 1.3: The C and G matrices	12
Section 1.4: DC Sweep of Vin from -10V to 10V	14
Section 1.5: The AC Case; Vout as a function of w	15
Section 1.6: The AC Case; Plotting Vo/Vi in dB	17
Section 1.7: The AC Case; Gain with Random Perturbations on C	18
Section 2: Transient Circuit Simulation	20
Section 2.1: Vin and Vout from Numerical Time Domain Solution	20
Section 2.2: Fourier Transform of the Output Solution	24
Section 3: Circuit Analysis Including Noise	25
Section 3.1: The Updated C Matrix	25
Section 3.2: Plotting Vout with Included Noise	28
Section 3.3: Varying Cn	30
Section 3.4: Varying Time Step	35
Section 4: Non-Linearity	39

Circuit Modeling

Keegan Mauger 101042551

Section 1: Revisiting PA7 and Assignment 3

In section 1, the MNA modeling done in PA7 and the monte-carlo/finite difference method code developed in assignment 3 are combined. First, assignment 3 is repurposed to find the resistance of R3 from PA7.

Section 1.1: Finding the Resistance of R3

The width of the bottleneck from assignment 3 was modified to find a resistance suggested by the TAs. First, the assignment code was re-run to find a plot of the average current vs Vin.

```
clear all
close all
clc
%set(0,'DefaultFigureWindowStyle','docked')
set(0,'defaultaxesfontsize',10)
set(0,'defaultaxesfontname','Times New Roman')
set(0,'DefaultLineWidth',0.5);

%-----
% Finite Difference Method Simulation
%-----
```

```
Zfac = 15e-9;
Vin = linspace(0.1,10,30);
Complete = linspace(0,100,30);
for J=1:length(Vin)
    %fprintf('\n%3.2f percent complete',Complete(J));
    % Fixed bottleneck of 0.2x10-7m
    % Solving V=V0 @ x=0 and V=0 @ x=L in region LxW
    % Implement funtion 'pbaspect' to fix Z aspect ratio
    clearvars -except Vin J Ix_total Iavg Zfac Complete

    Conc = 1e19;
    L = 200e-9;
    W = 100e-9;
    V0 = Vin(J);

    fMesh = 1;
    nx = fMesh*200;
    ny = fMesh*100;
    La = linspace(0,L,nx);
    Wa = linspace(0,W,ny);
    G = sparse(nx*ny);
    %V = sparse(nx,ny);
    F = sparse(1,nx*ny);

    Acond = 1; % background conductivity of region, low resistance
    Bcond = 1e-2; % Conductivity of boxes, highly resistive
    cMap = zeros(nx,ny);
    Lb = 40e-9;
    Wb = 40e-9;
    for u = 1:nx
        for v = 1:ny
            if (u >= 80 && u <= 120)
                if v >= 0 && v <= 40-1+J
                    cMap(u,v) = Bcond;
                elseif v >= 60+1-J && v <= 100
                    cMap(u,v) = Bcond;
                else
                    cMap(u,v) = Acond;
                end
            else
                cMap(u,v) = Acond;
            end
        end
    end

    for i = 1:nx %Iteration through length
        for j = 1:ny %Iteration through width
            n = j + (i-1)*ny;
```

```
if i == 1                % x=0 BCs
    G(n,:) = 0;
    G(n,n) = 1;
    F(n) = V0;
elseif i == nx           % x=1 BCs
    G(n,:) = 0;
    G(n,n) = 1;
    F(n) = 0;            %F(n)=0 sets z at final width to 0

% COMMENT BELOW FOR 1a
    %F(n) = 1;           %F(n)=1 sets z at final width to 1

elseif j == 1            % y=0 BCs
    nxm = j + (i-2)*ny;
    nxp = j + (i)*ny;
    nyp = j+1 + (i-1)*ny;

    rxm = (cMap(i,j) + cMap(i-1,j))/2;
    rxp = (cMap(i,j) + cMap(i+1,j))/2;
    ryp = (cMap(i,j) + cMap(i,j+1))/2;

    G(n,n) = -(rxm+rxp+ryp);
    G(n,nxm) = rxm;
    G(n,nxp) = rxp;
    G(n,nyp) = ryp;

elseif j == ny           % y=1 BCs
    nxm = j + (i-2)*ny;
    nxp = j + (i)*ny;
    nym = j-1 + (i-1)*ny;

    rxm = (cMap(i,j) + cMap(i-1,j))/2;
    rxp = (cMap(i,j) + cMap(i+1,j))/2;
    rym = (cMap(i,j) + cMap(i,j-1))/2;

    G(n,n) = -(rxm+rxp+rym);
    G(n,nxm) = rxm;
    G(n,nxp) = rxp;
    G(n,nym) = rym;

% COMMENT ABOVE FOR 1a

else
    nxm = j + (i-2)*ny;
    nxp = j + (i)*ny;
    nym = j-1 + (i-1)*ny;
    nyp = j+1 + (i-1)*ny;

    rxm = (cMap(i,j) + cMap(i-1,j))/2;
    rxp = (cMap(i,j) + cMap(i+1,j))/2;
    rym = (cMap(i,j) + cMap(i,j-1))/2;
    ryp = (cMap(i,j) + cMap(i,j+1))/2;
```

```
G(n,n) = -(rxm+rxp+rym+ryp);
G(n,nxm) = rxm;
G(n,nxp) = rxp;
G(n,nym) = rym;
G(n,nyp) = ryp;
end

end

end
% figure(1)
% spy(G)

V = G\F';

Vmap = zeros(nx,ny);
for i = 1:nx
    for j = 1:ny
        n = j + (i-1)*ny;
        Vmap(i,j) = V(n);
    end
end

for i = 1:nx
    for j = 1:ny
        if i == 1
            Ex(i, j) = (Vmap(i + 1, j) - Vmap(i, j));
        elseif i == nx
            Ex(i, j) = (Vmap(i, j) - Vmap(i - 1, j));
        else
            Ex(i, j) = (Vmap(i + 1, j) - Vmap(i - 1, j)) * 0.5;
        end
        if j == 1
            Ey(i, j) = (Vmap(i, j + 1) - Vmap(i, j));
        elseif j == ny
            Ey(i, j) = (Vmap(i, j) - Vmap(i, j - 1));
        else
            Ey(i, j) = (Vmap(i, j + 1) - Vmap(i, j - 1)) * 0.5;
        end
    end
end

Ex = -Ex;
Ey = -Ey;

eFlowx = cMap .* Ex;           %Jx
eFlowy = cMap .* Ey;           %Jy
C0 = sum(eFlowx(1, :));
Cnx = sum(eFlowx(nx, :));
Curr = (C0 + Cnx) * 0.5;

Ex = Ex';
Ey = Ey';
```

```
% figure(4)
% subplot(1, 2, 2), quiver(Ex, Ey);
% axis([0 nx 0 ny]);
% title('Electric Field Map')
% xlabel('Region Length')
% ylabel('Region Width')
% pbaspect([1 1 0.5])
% subplot(1, 2, 1), H = surf(La,Wa,Vmap');
% set(H, 'linestyle', 'none');
% %view(90, 270)
% title('Voltage Map')
% xlabel('Region Length')
% ylabel('Region Width')
% pbaspect([1 1 0.5])
% saveas(gcf,'Figure4')

% clearvars -except Ex Ey

%-----
% Beginning Monte Carlo Simulation
%-----

set(0,'DefaultFigureWindowStyle','docked')
set(0,'defaultaxesfontsize',10)
set(0,'defaultaxesfontname','Times New Roman')
set(0,'DefaultLineLineWidth', 0.5);

global C

C.q_0 = 1.60217653e-19;           % electron charge
C.hb = 1.054571596e-34;          % Dirac constant
C.h = C.hb * 2 * pi;             % Planck constant
C.m_0 = 9.10938215e-31;          % electron mass
C.kb = 1.3806504e-23;            % Boltzmann constant
C.eps_0 = 8.854187817e-12;       % vacuum permittivity
C.mu_0 = 1.2566370614e-6;        % vacuum permeability
C.c = 299792458;                 % speed of light
C.g = 9.80665;                   % metres (32.1740 ft) per s2
C.m_n = 0.26 * C.m_0;            % effective electron mass
C.am = 1.66053892e-27;           % atomic mass unit
C.T = 300;
C.vth = sqrt(2*C.kb * C.T / C.m_n);

temp = C.T;

SPECDIFF_BOUND = 0;

% figure(3)
% subplot(2,1,1);
% rectangle('Position',[0 0 200e-9 100e-9])
% hold on
```

```
% rectangle('Position',[0.8e-7 0 0.4e-7 0.4e-7])
% hold on
% rectangle('Position',[0.8e-7 0.6e-7 0.4e-7 0.4e-7])
% hold on

%-----
% Initializing Positions
%-----

N = 30000;          % Number of electrons
i = 0;
j = 0;

for i=1:N
    px(i) = 0 + (200e-9 - 0).*rand(1,1);
    py(i) = 0 + (100e-9 - 0).*rand(1,1);
    while (0.8e-7 <= px(i) && px(i) <= 1.2e-7) && (0 <= py(i) && py(i) <=
(0.4e-7 - Zfac) ) || ...
        (0.8e-7 <= px(i) && px(i) <= 1.2e-7) && ((0.6e-7 + Zfac) <=
py(i) && py(i) <= 1e-7)
        px(i) = 0 + (200e-9 - 0).*rand(1,1);
        py(i) = 0 + (100e-9 - 0).*rand(1,1);
    end
end

%-----
% Voltage Applied Across x-Dimension to Find Electric Field
%-----

V0x = Vin(J);
V0y = 0;
L = 200e-9;
W = 100e-9;
% E0x = V0x / L;
% E0y = V0y / W;
fMesh = 1;
nx = fMesh*200;
ny = fMesh*100;
% G = sparse(nx,ny);
% F = sparse(1,nx*ny);

La = linspace(0,L,nx);
Wa = linspace(0,W,ny);

deltax = L/nx;
deltay = W/ny;

Ex = Ex./deltax;
Ey = Ey./deltay;

% Emapx = zeros(ny,nx);
Emapx = Ex;
% Emapy = zeros(ny,nx);
Emapy = Ey;
```

```
% for i = 1:width(La)
%     for j = 1:width(Wa)
%         Emapx(j,i) = E0x;
%         Emapy(j,i) = E0y;
%     end
% end
% %surf(La,Wa,Emapx)
%
% Fex = abs(C.q_0*E0x);
% aex = Fex/C.m_n;
% Fey = abs(C.q_0*E0y);
% aey = Fey/C.m_n;

Fex = zeros(ny,nx);
aex = zeros(ny,nx);
Fey = zeros(ny,nx);
aey = zeros(ny,nx);

for i = 1:width(Wa)
    for j = 1:width(La)
        Fex(i,j) = abs(C.q_0*Emapx(i,j));
        aex(i,j) = Fex(i,j)/C.m_n;
        Fey(i,j) = abs(C.q_0*Emapy(i,j));
        aey(i,j) = Fey(i,j)/C.m_n;
    end
end

%-----
% Thermal Velocity and Direction
%-----

vth = C.vth;

for j=1:N
    vx(j) = (vth/sqrt(2))*randn();
    vy(j) = (vth/sqrt(2))*randn();
    vth_calc(j) = sqrt(vx(j)^2 + vy(j)^2);
end

t = 0;
T(1) = 0;
dt = 1e-14;      % time step

for l=1:N          %Scattering time step
    ndt(l) = dt;
end
P_scatt = 0;
Tmn = 0.2e-12;
```

```
px_prev = 0;
py_prev = 0;
T_prev = 0;
vx_total = 0;
vy_total = 0;

sampleidx = randi(N,10,1);
Ix = 0;
Jx = 0;
aex = aex';
aey = aey';

for t=2:1000
    vx_total = 0;
    vy_total = 0;
    for k=1:N

        rpx = 0;
        rpy = 0;
        if px(k) == 200e-9
            px(k) = 0;
            px_prev(k) = px(k);
        elseif px(k) == 0
            px(k) = 200e-9;
            px_prev(k) = px(k);
        else
            px(k) = px(k);
        end

        P_scat(k) = 1 - exp(-(dt/Tmn));
        if P_scat(k) > rand()
            vx(k) = (vth/sqrt(2))*randn();
            vy(k) = (vth/sqrt(2))*randn();
        else
            ndt(k) = ndt(k) + dt;
        end

        px_prev(k) = px(k);
        py_prev(k) = py(k);

        rpx = round(px(k)*1e9);
        if rpx == 0
            rpx = 1;
        end
        rpy = round(py(k)*1e9);
        if rpy == 0
            rpy = 1;
        end
    end
end
```



```
        px(k) = px(k) + vx(k)*dt + aex(rpx,rpy)*dt^2;           % Adding
acceleration
        vx(k) = vx(k) + aex(rpx,rpy)*dt;
        py(k) = py(k) + vy(k)*dt + aey(rpx,rpy)*dt^2;
        vy(k) = vy(k) + aey(rpx,rpy)*dt;

% Reflection on top and bottom borders
if py(k) >= 100e-9 || py(k) <= 0
    vy(k) = -vy(k);
    if py(k) >= 100e-9
        py(k) = 100e-9;
    end
    if py(k) <= 0
        py(k) = 0;
    end
end
% Reflection on bottom of upper box
if (py(k) >= (0.6e-7 + Zfac)) && (0.8e-7 <= px(k) && px(k) <=
1.2e-7)...
    && ( 0.8e-7 <= px_prev(k) && px_prev(k) <= 1.2e-7)
    if SPECDIFF_BOUND == 1
        vx(k) = (vth/sqrt(2))*randn();
        vy(k) = (vth/sqrt(2))*randn();
    else
        vy(k) = -vy(k);
    end
    py(k) = 0.601e-7 + Zfac;
    %end
    % Reflection on top of lower box
elseif (py(k) <= 0.4e-7 - Zfac) && (0.8e-7 <= px(k) && px(k) <=
1.2e-7)...
    && (0.8e-7 <= px_prev(k) && px_prev(k) <= 1.2e-7)
    if SPECDIFF_BOUND == 1
        vx(k) = (vth/sqrt(2))*randn();
        vy(k) = (vth/sqrt(2))*randn();
    else
        vy(k) = -vy(k);
    end
    py(k) = 0.399e-7 - Zfac;
    %end
    % Reflection on left of lower box
elseif (0 <= py(k) && py(k) <= 0.4e-7 - Zfac) && (0.8e-7 <= px(k)
&& px(k) <= 1e-7)
    if SPECDIFF_BOUND == 1
        vx(k) = (vth/sqrt(2))*randn();
        vy(k) = (vth/sqrt(2))*randn();
    else
        vx(k) = -vx(k);
    end
    px(k) = 0.799e-7;
    %end
    % Reflection on right of lower box
```

```

        elseif (0 <= py(k) && py(k) <= 0.4e-7 - Zfac) && (1e-7 <= px(k) &&
px(k) <= 1.2e-7)
            if SPECDIFF_BOUND == 1
                vx(k) = (vth/sqrt(2))*randn();
                vy(k) = (vth/sqrt(2))*randn();
            else
                vx(k) = -vx(k);
            end
            px(k) = 1.201e-7;
            %end
            % Reflection on left of upper box
        elseif (0.6e-7 + Zfac <= py(k) && py(k) <= 1e-7) && (0.8e-7 <=
px(k) && px(k) <= 1e-7)
            if SPECDIFF_BOUND == 1
                vx(k) = (vth/sqrt(2))*randn();
                vy(k) = (vth/sqrt(2))*randn();
            else
                vx(k) = -vx(k);
            end
            px(k) = 0.799e-7;
            %end
            % Reflection on right of upper box
        elseif (0.6e-7 + Zfac <= py(k) && py(k) <= 1e-7) && (1e-7 <= px(k)
&& px(k) <= 1.2e-7)
            if SPECDIFF_BOUND == 1
                vx(k) = (vth/sqrt(2))*randn();
                vy(k) = (vth/sqrt(2))*randn();
            else
                vx(k) = -vx(k);
            end
            px(k) = 1.201e-7;
        end

        % x-axis transition
        if px(k) > 200e-9
            px(k) = 200e-9;
            %           px_prev(k) = px(k);
        elseif px(k) < 0
            px(k) = 0;
            %           px_prev(k) = px(k);
        else
            px(k) = px(k);
        end

        v(k) = sqrt(vx(k)^2 + vy(k)^2);
        v2(k) = v(k).*v(k);

        vx_total = vx_total + vx(k);           % Drift velocity x
        vy_total = vy_total + vy(k);           % Drift velocity y
    end
    vx_total_alt = sum(vx);

```

```

vx_drift = 1/N * vx_total;
vy_drift = 1/N * vy_total;
Jx = C.q_0 * Conc * vx_drift;    %Concentration = 1e19 per m^-2
Ix_prev = Ix;
Ix = Jx * W;
Ix_total(t) = Ix;


end

Iavg(J) = mean(Ix_total);
%bottleneck(J) = 20e-9 - (2*g) + 2e-9;

end

figure(1)
plot(Vin,Iavg)
xlabel('Input Voltage (V)')
ylabel('Average Current (A)')
title('Average Current VS Input Voltage')
saveas(gcf,'Figure1')

```

 

Section 1.2: Calculating the resistance of R3

The solved resistance of R3 was then found to be approximately 51.32 ohms, found through a linear fit of the plot.

```

linFit = polyfit(Vin,Iavg,1);
G3 = linFit(1);

```

```
R3 = 1/G3;
```

```
fprintf('\n\nThe resistance of R3 is %f ohms.',R3);  
clearvars -except R3
```

The resistance of R3 is 51.312778 ohms.

Section 1.3: The C and G matrices

Using code from PA7, the C and G matrices of the circuit were formed and are displayed below.

```
%-----  
% Reusing Modified Nodal Analysis Code for Circuit - DC Case  
%-----  
  
global G b C  
nodes = 6;  
G = sparse(nodes,nodes);  
C = sparse(nodes,nodes);  
b = sparse(nodes,1);  
  
% MNA setup  
Vin = 1;  
Vprobe = 0;  
R1 = 1;  
R2 = 2;  
%R3 = 10; %R3 found in part 1  
R4 = 0.1;  
R5 = 1000;  
C1 = 0.25;  
L1 = 0.2;  
alpha = 100;  
  
cap(1,2,C1);  
res(1,2,R1);  
res(2,0,R2);  
res(3,6,R3);  
res(4,5,R4);  
res(5,0,R5);  
xr = vol(6,0,Vprobe);  
ind(2,3,L1);  
vol(1,0,Vin);  
vcvs(4,0,xr,0,alpha);  
  
w = 0;  
s = j*w;  
  
A = G + s*C;  
A0 = full(A);  
G0 = full(G);  
C0 = full(C);  
  
fprintf('\n\nThe G matrix is given as:\n');
```

```
disp(G0);

fprintf('\nThe C matrix is given as:\n');
disp(C0);
```

The G matrix is given as:
Columns 1 through 7

1.0000	-1.0000	0	0	0	0	0
-1.0000	1.5000	0	0	0	0	0
0	0	0.0195	0	0	-0.0195	0
0	0	0	10.0000	-10.0000	0	0
0	0	0	-10.0000	10.0010	0	0
0	0	-0.0195	0	0	0.0195	1.0000
0	0	0	0	0	1.0000	0
0	1.0000	-1.0000	0	0	0	0
1.0000	0	0	0	0	0	0
0	0	0	1.0000	0	0	-100.0000

Columns 8 through 10

0	1.0000	0
1.0000	0	0
-1.0000	0	0
0	0	1.0000
0	0	0
0	0	0
0	0	0
0	0	0
0	0	0
0	0	0

The C matrix is given as:
Columns 1 through 7

0.2500	-0.2500	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0

Columns 8 through 10

0	0	0
0	0	0
0	0	0
0	0	0

0	0	0
0	0	0
0	0	0
-0.2000	0	0
0	0	0
0	0	0

Section 1.4: DC Sweep of Vin from -10V to 10V


Next, the value of Vin (at node 1) was swept from -10V to 10V and the resulting output at node 3 and the output were plotted.

```
V0 = linspace(-10,10,21);
b0 = sparse((width(G)),width(V0));
for i = 1:width(V0)
    b0(9,i) = V0(i);
end

x = sparse((width(G)),width(V0));

for j = 1:width(V0)
    x(:,j) = (G + s*C) \ b0(:,j);
end

figure(2)
plot(V0,x(5,:))
hold on
plot(V0,x(3,:))
grid on
axis([-10 10 -100 100])
title('Vout vs Vin')
xlabel('Vin')
ylabel('Vout')
legend('Vout','V3')
saveas(gcf,'Figure2')
hold off
```

 

Section 1.5: The AC Case; Vout as a function of ω

Vout was then plotted as a function of ω (omega), where omega was swept from 0Hz to 100Hz over 100 points.

```
%-----
% AC Case
%-----

clearvars -except R3
global G b C
nodes = 6;
G = sparse(nodes,nodes);
C = sparse(nodes,nodes);
b = sparse(nodes,1);

% MNA setup
Vin = 1;
Vprobe = 0;
R1 = 1;
R2 = 2;
R3 = 10;
R4 = 0.1;
R5 = 1000;
C1 = 0.25;
L1 = 0.2;
alpha = 100;

cap(1,2,C1);
res(1,2,R1);
```

```
res(2,0,R2);
res(3,6,R3);
res(4,5,R4);
res(5,0,R5);
xr = vol(6,0,Vprobe);
ind(2,3,L1);
vol(1,0,Vin);
vcvs(4,0,xr,0,alpha);

w = linspace(0,100,100);
s = j*w;


% A = G + s.*C;
% A0 = full(A);

%V0 = linspace(-10,10,21);
% b0 = sparse((width(G)),width(w));
% for i = 1:width(w)
%     b0(6,i) = V0(i);
% end

% x = (G + s*C) \ b;
x = sparse((width(G)),width(w));

for i = 1:width(w)
    x(:,i) = (G + s(i)*C) \ b;
end


figure(3)
plot(w,abs(x(5,:)))
%hold on
%plot(w,abs(x(3,:)))
grid on
title('|Vout| vs Frequency')
xlabel('Frequency (Hz)')
ylabel('Voltage (V)')
%legend('Vout','V3')
saveas(gcf,'Figure3')
hold off
```

 Section 1.6: The AC Case; Plotting V_o/V_i in dB

The gain of V_{out} over V_{in} was also plotted, in dB.

```
mag = abs(x(5,:)./x(1,:));  
gain = mag2db(mag);  
figure(4)  
plot(w,gain)  
grid on  
title('Gain vs Frequency')  
ylabel('Gain (dB)')  
xlabel('Frequency (Hz)')  
saveas(gcf, 'Figure4')
```

 

Section 1.7: The AC Case; Gain with Random Perturbations on C

Setting the capacitor C to have a normal distribution of random perturbations with a standard deviation of 0.05 and $w = \pi$, the gain and value of C was plotted as a histogram.

```
%-----
% AC Case - Normal Perturbations on C
%-----

clearvars -except R3
global G b C
nodes = 6;
G = sparse(nodes,nodes);
C = sparse(nodes,nodes);
b = sparse(nodes,1);

% MNA setup
Vin = 1;
Vprobe = 0;
R1 = 1;
R2 = 2;
R3 = 10;
R4 = 0.1;
R5 = 1000;
C1 = 0.25;
L1 = 0.2;
alpha = 100;

cap(1,2,C1);
```

```
res(1,2,R1);
res(2,0,R2);
res(3,6,R3);
res(4,5,R4);
res(5,0,R5);
xr = vol(6,0,Vprobe);
ind(2,3,L1);
vol(1,0,Vin);
vcvs(4,0,xr,0,alpha);


w = pi;
s = j*w;
std = 0.05;
mu = C1;
numR = 1000;
r = normrnd(mu,std,1,numR);

C0 = zeros(width(G),length(G),numR);
for i = 1:width(r)
    C(1:2,1:2) = 0;
    cap(1,2,r(i));
    C0(:, :, i) = C;
end

x = sparse((width(G)),numR);
for i = 1:numR
    x(:,i) = (G + s*C0(:, :, i)) \ b;
end

mag = abs(x(5,:)./x(1,:));
gain = mag2db(mag);

figure(5)
subplot(1,2,1);
hist(r)
title('Histogram of C, Normal Distribution')
xlabel('C')
ylabel('Number')
subplot(1,2,2);
hist(mag,10)
title('Histogram of Gain, Normal Distribution')
xlabel('Gain (V/V)')
ylabel('Number')
saveas(gcf,'Figure5')
```

 

Section 2: Transient Circuit Simulation

In Section 2, the time frequency domain solution method of the circuit would be replaced by a time domain solution, using the Backwards Euler method. Additionally, the circuit takes the form of a series bandpass RLC circuit, due to the series inductance and capacitance. The frequency response would be expected to have a high peak magnitude where the frequency passes through the filter.

Section 2.1: Vin and Vout from Numerical Time Domain Solution

Using the Backwards Euler method, the numerical solution of the circuit was found for three inputs: a step function, a sin function, and a gaussian function. The transient analysis of the output was then plotted.

```
clearvars -except R3
% close all
% clc
%set(0,'DefaultFigureWindowStyle','docked')
set(0,'defaultaxesfontsize',10)
set(0,'defaultaxesfontname','Times New Roman')
set(0,'DefaultLineLineWidth', 0.5);
```

```
%-----
% Modified Nodal Analysis - Transient Analysis
%-----
```

```
global G b C
nodes = 6;
outNode = 5;
G = sparse(nodes,nodes);
```

```
C = sparse(nodes,nodes);
b = sparse(nodes,1);

N = 1000; %num points
t_vec_1 = linspace(0,1,N);
t_vec_2 = linspace(0+0.06,1-0.06,1000-120);
t = 0;
u_t = 0;
v_t = 0;
w_t = 0;

f = 1/0.03;
A1 = 1;
w = 2*pi*f;

X = t_vec_2;
A2 = 1;
mu = 0.5;
sigma = 0.03;
delay = 0.06;

gaussian = A2*exp(-((X-mu).^2/(2*sigma.^2)));

z = 0;

for k = 1:numel(t_vec_1)
    t = t_vec_1(k);
    %input 1
    if t < 0.03
        u_t(k) = 0;
    else
        u_t(k) = 1;
    end
    %input 2
    v_t(k) = A1*sin(w*t);
    %input 3
    if t < 0.06
        w_t(k) = 0;
    elseif t >= 0.06 && t < 0.94
        w_t(k) = gaussian(k-60);
    elseif t >= 0.94
        w_t(k) = 0;
    else
        w_t(k) = 0;
    end
end

% plot(t_vec_1,u_t);
% hold on
% plot(t_vec_1,v_t);
% plot(t_vec_1,w_t);
```

```
% hold off

%-----
% MNA setup
%-----
Vin = 1;
Vprobe = 0;
R1 = 1;
R2 = 2;
% R3 = 50;
%R3 = 123.346641;
R4 = 0.1;
R5 = 1000;
C1 = 0.25;
L1 = 0.2;
alpha = 100;

cap(1,2,C1);
res(1,2,R1);
res(2,0,R2);
res(3,6,R3);
res(4,5,R4);
res(5,0,R5);
xr = vol(6,0,Vprobe);
ind(2,3,L1);
vol(1,0,Vin);
vcvs(4,0,xr,0,alpha);

b1 = b*u_t;
b2 = b*v_t;
b3 = b*w_t;

%-----
% FDM Solution: Backwards Euler with Timestep 0.001
%-----
h = 0.001;
x = sparse(width(G),numel(t_vec_1));
C_h = C*(1/h);

for n=1:1000
    if n == 1000
        break;
    end
    BE_LHS = C_h + G;
    BE_RHS = C_h*x(:,n) + b1(:,n+1);
    [L, U, P, Q]= lu( sparse(BE_LHS) , 0.1 );
    Z = L \ (P* sparse(BE_RHS));
    Y = U \ Z;
    x(:,n+1) = Q*Y;
end
```

```
end
BE1 = x;
for n=1:1000
    if n == 1000
        break;
    end
    BE_LHS = C_h + G;
    BE_RHS = C_h*x(:,n) + b2(:,n+1);
    [L, U, P, Q]= lu( sparse(BE_LHS) , 0.1 );
    Z = L \ (P* sparse(BE_RHS));
    Y = U \ Z;
    x(:,n+1) = Q*Y;
end
BE2 = x;
for n=1:1000
    if n == 1000
        break;
    end
    BE_LHS = C_h + G;
    BE_RHS = C_h*x(:,n) + b3(:,n+1);
    [L, U, P, Q]= lu( sparse(BE_LHS) , 0.1 );
    Z = L \ (P* sparse(BE_RHS));
    Y = U \ Z;
    x(:,n+1) = Q*Y;
end
BE3 = x;

figure(6)
subplot(3,1,1);
plot(t_vec_1, u_t, 'LineWidth',1);
hold on;
plot(t_vec_1, BE1(outNode,:), 'LineStyle','-.', 'color','r','LineWidth',1);
title('Vin and Vout for Step Function Input')
ylabel('Voltage (V)')
xlabel('Time (s)')
legend('Vin', 'Vout')
hold off


subplot(3,1,2);
plot(t_vec_1, v_t, 'LineWidth',1);
hold on;
plot(t_vec_1, BE2(outNode,:), 'LineStyle','-.', 'color','r','LineWidth',1);
title('Vin and Vout for Sin Function Input')
ylabel('Voltage (V)')
xlabel('Time (s)')
legend('Vin', 'Vout')
hold off

subplot(3,1,3);
plot(t_vec_1, w_t, 'LineWidth',1);
hold on;
plot(t_vec_1, BE3(outNode,:), 'LineStyle','-.', 'color','r','LineWidth',1);
```

```

title('Vin and Vout for Gaussian Function Input')
ylabel('Voltage (V)')
xlabel('Time (s)')
legend('Vin', 'Vout')
hold off
saveas(gcf, 'Figure6')

```

 

Section 2.2: Fourier Transform of the Output Solution

The Fourier transform of the output signal was then plotted for each of the three inputs. It was also noted that an increase in timestep for the Backwards Euler solution led to a decrease in accuracy of the solution.

```

Fs = 1/h;
dF = Fs/N;
f = -Fs/2:dF:FsWithoutZero - dF;

%F_vec_1 = 1./t_vec_1;
figure(7)
subplot(3,1,1);
fullBE1 = full(BE1(outNode,:));
FT1 = fft(fullBE1);
plot(f,fftshift(abs(FT1)))
title('Fourier Transform of Vout with Step Input')
ylabel('Magnitude')
xlabel('Frequency (Hz)')

subplot(3,1,2);
fullBE2 = full(BE2(outNode,:));
FT2 = fft(fullBE2);

```




```

plot(f,fftshift(abs(FT2)))
title('Fourier Transform of Vout with Sinusoidal Input')
ylabel('Magnitude')
xlabel('Frequency (Hz)')

subplot(3,1,3);
fullBE3 = full(BE3(outNode,:));
FT3 = fft(fullBE3);
plot(f,fftshift(abs(FT3)))
title('Fourier Transform of Vout with Gaussian Input')
ylabel('Magnitude')
xlabel('Frequency (Hz)')
saveas(gcf,'Figure7')

```

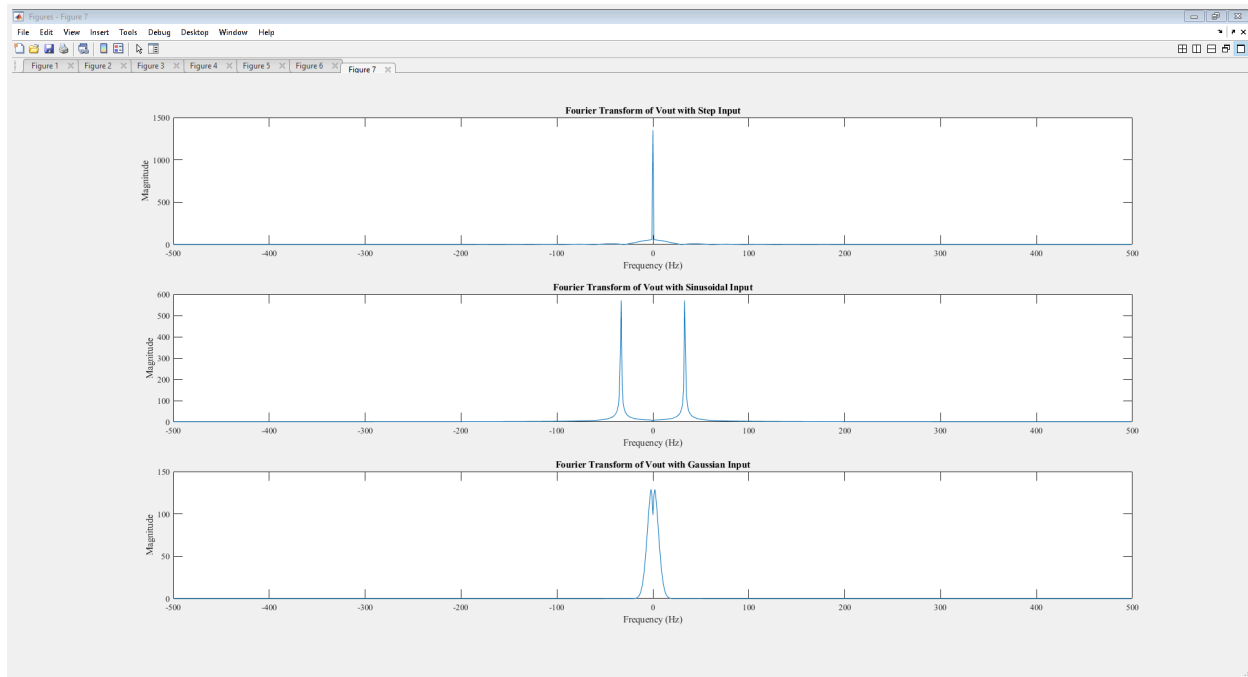

Section 3: Circuit Analysis Including Noise

Following the circuit analysis, a noise source and capacitance was then added in parallel with the resistor R3.

Section 3.1: The Updated C Matrix

The addition of the noise capacitor Cn resulted in an update to the C matrix. The updated matrix is given below.

```

clearvars -except R3
% close all
% clc
%set(0,'DefaultFigureWindowStyle','docked')
set(0,'defaultaxesfontsize',10)
set(0,'defaultaxesfontname','Times New Roman')
set(0,'DefaultLineLineWidth', 0.5);

```

```
%-----
```

```
% Modified Nodal Analysis - Transient Analysis
```

```
%-----
```

```
global G b C
```

```
nodes = 6;
```

```
outNode = 5;
```

```
inNode = 9;
```

```
N = 1000; %num points
```

```
G = sparse(nodes,nodes);
```

```
C = sparse(nodes,nodes);
```

```
b = sparse(nodes,1);
```

```
t_vec_1 = linspace(0,1,1000);
```

```
t_vec_2 = linspace(0+0.06,1-0.06,1000-120);
```

```
t = 0;
```

```
u_t = 0;
```

```
v_t = 0;
```

```
w_t = 0;
```

```
f = 1/0.03;
```

```
A1 = 1;
```

```
w = 2*pi*f;
```

```
X = t_vec_2;
```

```
A2 = 1;
```

```
mu = 0.5;
```

```
sigma = 0.03;
```

```
delay = 0.06;
```

```
gaussian = A2*exp(-((X-mu).^2/(2*sigma.^2)));
```

```
z = 0;
```

```
for k = 1:numel(t_vec_1)
```

```
    t = t_vec_1(k);
```

```
    %input 1
```

```
    if t < 0.03
```

```
        u_t(k) = 0;
```

```
    else
```

```
        u_t(k) = 1;
```

```
    end
```

```
    %input 2
```

```
    v_t(k) = A1*sin(w*t);
```

```
    %input 3
```

```
    if t < 0.06
```

```
        w_t(k) = 0;
```

```
    elseif t >= 0.06 && t < 0.94
```

```
        w_t(k) = gaussian(k-60);
```

```
    elseif t >= 0.94
```

```
        w_t(k) = 0;
```

```
    else
```

```
        w_t(k) = 0;
```

end

end

```
% plot(t_vec_1,u_t);
% hold on
% plot(t_vec_1,v_t);
% plot(t_vec_1,w_t);
% hold off
```

```
%-----
% MNA setup
%-----
Vin = 1;
Vprobe = 0;
R1 = 1;
R2 = 2;
R3 = 123.346641;
R3 = 50;
R4 = 0.1;
R5 = 1000;
C1 = 0.25;
L1 = 0.2;
alpha = 100;
In = 0.001;
Cn = 0.00001;

cap(1,2,C1);
res(1,2,R1);
res(2,0,R2);
res(3,6,R3);
res(4,5,R4);
res(5,0,R5);
xr = vol(6,0,Vprobe);
ind(2,3,L1);
vol(1,0,Vin);
vcvs(4,0,xr,0,alpha);
cur(4,0,6);
cap(4,0,Cn);

fullC = full(C);
fprintf('\nThe updated C matrix is given by:\n');
disp(fullC);
```

*The updated C matrix is given by:
Columns 1 through 7*

0.2500	-0.2500	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0.0000	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0

Columns 8 through 10

0	0	0
0	0	0
0	0	0
0	0	0
0	0	0
0	0	0
0	0	0
0	0	0
-0.2000	0	0
0	0	0
0	0	0

Section 3.2: Plotting Vout with Included Noise

The time domain and frequency domain plots of Vout with included noise were then formed.

```
% b1 = b*u_t;
% b2 = b*v_t;
b3 = zeros(10,1000);
b3(inNode,:) = w_t;

% r = normrnd(mu,std,1000);
for i = 1:1000
    r = In*randn();
    b3(4,i) = r;
    b3(6,i) = -r;
    %b3(4,i) = 1;
end
% make b*wt and In into 2 different things

%-----
% FDM Solution: Backwards Euler with Timestep 0.001
%-----
h = 0.001;
x = sparse(width(G),numel(t_vec_1));
C_h = C*(1/h);


for n=1:1000
    if n == 1000
        break;
    end
end
```

```
end
BE_LHS = C_h + G;
BE_RHS = C_h*x(:,n) + b3(:,n+1);
[L, U, P, Q]= lu( sparse(BE_LHS) , 0.1 );
Z = L \ (P* sparse(BE_RHS));
Y = U \ Z;
x(:,n+1) = Q*Y;
end
BE3 = x;

Fs = 1/h;
dF = Fs/N;
f = -Fs/2:dF:Fs/2 - dF;

figure(8)
subplot(2,1,1);
plot(t_vec_1, w_t, 'LineWidth',1);
hold on;
plot(t_vec_1, BE3(outNode,:), 'LineStyle','-.', 'color','r','LineWidth',1);
title('Vin and Vout for Gaussian Function Input')
ylabel('Voltage (V)')
xlabel('Time (s)')
legend('Vin', 'Vout')
hold off

subplot(2,1,2);
fullBE3 = full(BE3(outNode,:));
FT3 = fft(fullBE3);
plot(f,fftshift(abs(FT3)))
title('Fourier Transform of Vout with Noise')
ylabel('Magnitude')
xlabel('Frequency (Hz)')
saveas(gcf, 'Figure8')
```

 

Section 3.3: Varying Cn

Next, Cn was changed between 3 different values of 0.0001, 0.00001, and 0.000001 Farads to view the effects on the response. It was found that the capacitance had a large effect on the non-noise voltage, but minimal effect on the noise itself.

```
clearvars -except R3
% close all
% clc
%set(0,'DefaultFigureWindowStyle','docked')
set(0,'defaultaxesfontsize',10)
set(0,'defaultaxesfontname','Times New Roman')
set(0,'DefaultLineLineWidth', 0.5);
```

```
H = [0.0001,0.00001,0.000001];
for J = 1:3
clearvars -except J H R3 BE3 N
%-----
% Modified Nodal Analysis - Transient Analysis
%-----
```

```
global G b C
nodes = 6;
outNode = 5;
inNode = 9;
N = 1000; %num points
G = sparse(nodes,nodes);
C = sparse(nodes,nodes);
b = sparse(nodes,1);
```

```
t_vec_1 = linspace(0,1,1000);
t_vec_2 = linspace(0+0.06,1-0.06,1000-120);
t = 0;
u_t = 0;
v_t = 0;
w_t = 0;

f = 1/0.03;
A1 = 1;
w = 2*pi*f;

X = t_vec_2;
A2 = 1;
mu = 0.5;
sigma = 0.03;
delay = 0.06;

gaussian = A2*exp(-((X-mu).^2/(2*sigma.^2)));

z = 0;

for k = 1:numel(t_vec_1)
    t = t_vec_1(k);
    %input 1
    if t < 0.03
        u_t(k) = 0;
    else
        u_t(k) = 1;
    end
    %input 2
    v_t(k) = A1*sin(w*t);
    %input 3
    if t < 0.06
        w_t(k) = 0;
    elseif t >= 0.06 && t < 0.94
        w_t(k) = gaussian(k-60);
    elseif t >= 0.94
        w_t(k) = 0;
    else
        w_t(k) = 0;
    end
end

% plot(t_vec_1,u_t);
% hold on
% plot(t_vec_1,v_t);
% plot(t_vec_1,w_t);
% hold off
```

```
%-----  
% MNA setup  
%-----  
Vin = 1;  
Vprobe = 0;  
R1 = 1;  
R2 = 2;  
%R3 = 123.346641;  
% R3 = 50;  
R4 = 0.1;  
R5 = 1000;  
C1 = 0.25;  
L1 = 0.2;  
alpha = 100;  
In = 0.001;  
Cn = H(J);  
  
cap(1,2,C1);  
res(1,2,R1);  
res(2,0,R2);  
res(3,6,R3);  
res(4,5,R4);  
res(5,0,R5);  
xr = vol(6,0,Vprobe);  
ind(2,3,L1);  
vol(1,0,Vin);  
vcvs(4,0,xr,0,alpha);  
cur(4,0,6);  
cap(4,0,Cn);  
  
% b1 = b*u_t;  
% b2 = b*v_t;  
b3 = zeros(10,1000);  
b3(inNode,:) = w_t;  
  
% r = normrnd(mu,std,1000);  
for i = 1:1000  
    r = In*randn();  
    b3(4,i) = r;  
    b3(6,i) = -r;  
    %b3(4,i) = 1;  
end  
% make b*wt and In into 2 different things  
  
%-----  
% FDM Solution: Backwards Euler with Timestep 0.001  
%-----  
h = H(J);  
x = sparse(width(G),numel(t_vec_1));
```

```
C_h = C*(1/h);

for n=1:1000
    if n == 1000
        break;
    end
    BE_LHS = C_h + G;
    BE_RHS = C_h*x(:,n) + b3(:,n+1);
    [L, U, P, Q]= lu( sparse(BE_LHS) , 0.1 );
    Z = L \ (P* sparse(BE_RHS));
    Y = U \ Z;
    x(:,n+1) = Q*Y;
end
BE3{J} = x;

end

Fs = 1/0.001;
dF = Fs/N;
f = -Fs/2:dF:Fs/2 - dF;

S1 = BE3{1};
S2 = BE3{2};
S3 = BE3{3};

figure(9)
subplot(2,3,1);
plot(t_vec_1, w_t, 'LineWidth',1)
hold on;
plot(t_vec_1, S1(outNode,:), 'LineStyle', '-.', 'color', 'r', 'LineWidth',1);
title('Vin and Vout with Noise, Cn = 0.0001F')
ylabel('Voltage (V)')
xlabel('Time (s)')
legend('Vin', 'Vout')
hold off

subplot(2,3,2);
plot(t_vec_1, w_t, 'LineWidth',1)
hold on;
plot(t_vec_1, S2(outNode,:), 'LineStyle', '-.', 'color', 'r', 'LineWidth',1);
title('Vin and Vout with Noise, Cn = 0.00001F')
ylabel('Voltage (V)')
xlabel('Time (s)')
legend('Vin', 'Vout')
hold off

subplot(2,3,3);
plot(t_vec_1, w_t, 'LineWidth',1)
hold on;
plot(t_vec_1, S3(outNode,:), 'LineStyle', '-.', 'color', 'r', 'LineWidth',1);
title('Vin and Vout with Noise, Cn = 0.000001F')
ylabel('Voltage (V)')
xlabel('Time (s)')
legend('Vin', 'Vout')
```

```


hold off

subplot(2,3,4);
fullS1 = full(S1(outNode,:));
FTS1 = fft(fullS1);
plot(f,fftshift(abs(FTS1)))
title('FT of Vout with Noise, Cn = 0.0001F')
ylabel('Magnitude')
xlabel('Frequency (Hz)')
hold off

subplot(2,3,5);
fullS2 = full(S2(outNode,:));
FTS2 = fft(fullS2);
plot(f,fftshift(abs(FTS2)))
title('FT of Vout with Noise, Cn = 0.00001F')
ylabel('Magnitude')
xlabel('Frequency (Hz)')
hold off

subplot(2,3,6);
fullS3 = full(S3(outNode,:));
FTS3 = fft(fullS3);
plot(f,fftshift(abs(FTS3)))
title('FT of Vout with Noise, Cn = 0.000001F')
ylabel('Magnitude')
xlabel('Frequency (Hz)')
saveas(gcf,'Figure9')
hold off

```

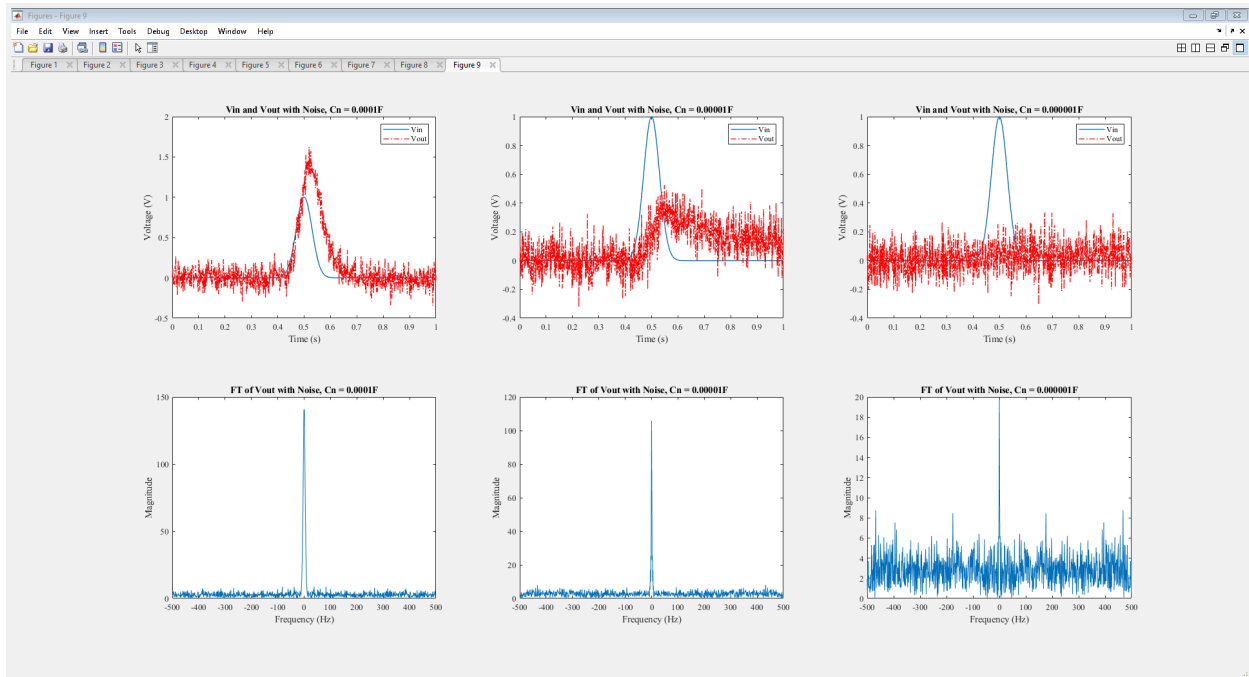

Section 3.4: Varying Time Step

Finally, the time step was varied between 0.01s and 0.001s, and the resulting plots were found. It was seen that a larger time step resulted in a less accurate solution, as expected.

```
clearvars -except R3
% close all
% clc
%set(0,'DefaultFigureWindowStyle','docked')
set(0,'defaultaxesfontsize',10)
set(0,'defaultaxesfontname','Times New Roman')
set(0,'DefaultLineLineWidth', 0.5);

H = [0.01, 0.001];
for J = 1:2
clearvars -except J H R3 BE3 N
%-----
% Modified Nodal Analysis - Transient Analysis
%-----

global G b C
nodes = 6;
outNode = 5;
inNode = 9;
N = 1000; %num points
G = sparse(nodes,nodes);
C = sparse(nodes,nodes);
b = sparse(nodes,1);

t_vec_1 = linspace(0,1,1000);
t_vec_2 = linspace(0+0.06,1-0.06,1000-120);
t = 0;
u_t = 0;
v_t = 0;
w_t = 0;

f = 1/0.03;
A1 = 1;
w = 2*pi*f;

X = t_vec_2;
A2 = 1;
mu = 0.5;
sigma = 0.03;
delay = 0.06;

gaussian = A2*exp(-((X-mu).^2/(2*sigma.^2)));

z = 0;

for k = 1:numel(t_vec_1)
```

```
t = t_vec_1(k);
%input 1
if t < 0.03
    u_t(k) = 0;
else
    u_t(k) = 1;
end
%input 2
v_t(k) = A1*sin(w*t);
%input 3
if t < 0.06
    w_t(k) = 0;
elseif t >= 0.06 && t < 0.94
    w_t(k) = gaussian(k-60);
elseif t >= 0.94
    w_t(k) = 0;
else
    w_t(k) = 0;
end

end

% plot(t_vec_1,u_t);
% hold on
% plot(t_vec_1,v_t);
% plot(t_vec_1,w_t);
% hold off

%-----
% MNA setup
%-----
Vin = 1;
Vprobe = 0;
R1 = 1;
R2 = 2;
%R3 = 123.346641;
% R3 = 50;
R4 = 0.1;
R5 = 1000;
C1 = 0.25;
L1 = 0.2;
alpha = 100;
In = 0.001;
Cn = 0.00001;

cap(1,2,C1);
res(1,2,R1);
res(2,0,R2);
```

```
res(3,6,R3);
res(4,5,R4);
res(5,0,R5);
xr = vol(6,0,Vprobe);
ind(2,3,L1);
vol(1,0,Vin);
vcvs(4,0,xr,0,alpha);
cur(4,0,6);
cap(4,0,Cn);

% b1 = b*u_t;
% b2 = b*v_t;
b3 = zeros(10,1000);
b3(inNode,:) = w_t;

% r = normrnd(mu,std,1000);
for i = 1:1000
    r = In*randn();
    b3(4,i) = r;
    b3(6,i) = -r;
    %b3(4,i) = 1;
end
% make b*wt and In into 2 different things

%-----
% FDM Solution: Backwards Euler with Timestep 0.001
%-----
h = H(J);
x = sparse(width(G),numel(t_vec_1));
C_h = C*(1/h);

for n=1:1000
    if n == 1000
        break;
    end
    BE_LHS = C_h + G;
    BE_RHS = C_h*x(:,n) + b3(:,n+1);
    [L, U, P, Q]= lu( sparse(BE_LHS) , 0.1 );
    Z = L \ (P* sparse(BE_RHS));
    Y = U \ Z;
    x(:,n+1) = Q*Y;
end
BE3{J} = x;

end

Fs = 1/0.001;
dF = Fs/N;
f = -Fs/2:dF:Fs/2 - dF;


S1 = BE3{1};
S2 = BE3{2};
```

```
figure(10)
subplot(2,2,1);
plot(t_vec_1, w_t, 'LineWidth',1)
hold on;
plot(t_vec_1, S1(outNode,:), 'LineStyle', '-.', 'color', 'r', 'LineWidth',1);
title('Vin and Vout for Gaussian Function Input with Noise, Timestep = 0.01s')
ylabel('Voltage (V)')
xlabel('Time (s)')
legend('Vin', 'Vout')
hold off

subplot(2,2,2);
plot(t_vec_1, w_t, 'LineWidth',1)
hold on;
plot(t_vec_1, S2(outNode,:), 'LineStyle', '-.', 'color', 'r', 'LineWidth',1);
title('Vin and Vout for Gaussian Function Input with Noise, Timestep =
      0.001s')
ylabel('Voltage (V)')
xlabel('Time (s)')
legend('Vin', 'Vout')
hold off

subplot(2,2,3);
fullS1 = full(S1(outNode,:));
FTS1 = fft(fullS1);
plot(f,fftshift(abs(FTS1)))
title('Fourier Transform of Vout with Noise, Timestep = 0.01s')
ylabel('Magnitude')
xlabel('Frequency (Hz)')
hold off

subplot(2,2,4);
fullS2 = full(S2(outNode,:));
FTS2 = fft(fullS2);
plot(f,fftshift(abs(FTS2)))
title('Fourier Transform of Vout with Noise, Timestep = 0.001s')
ylabel('Magnitude')
xlabel('Frequency (Hz)')
saveas(gcf, 'Figure10')
hold off
```

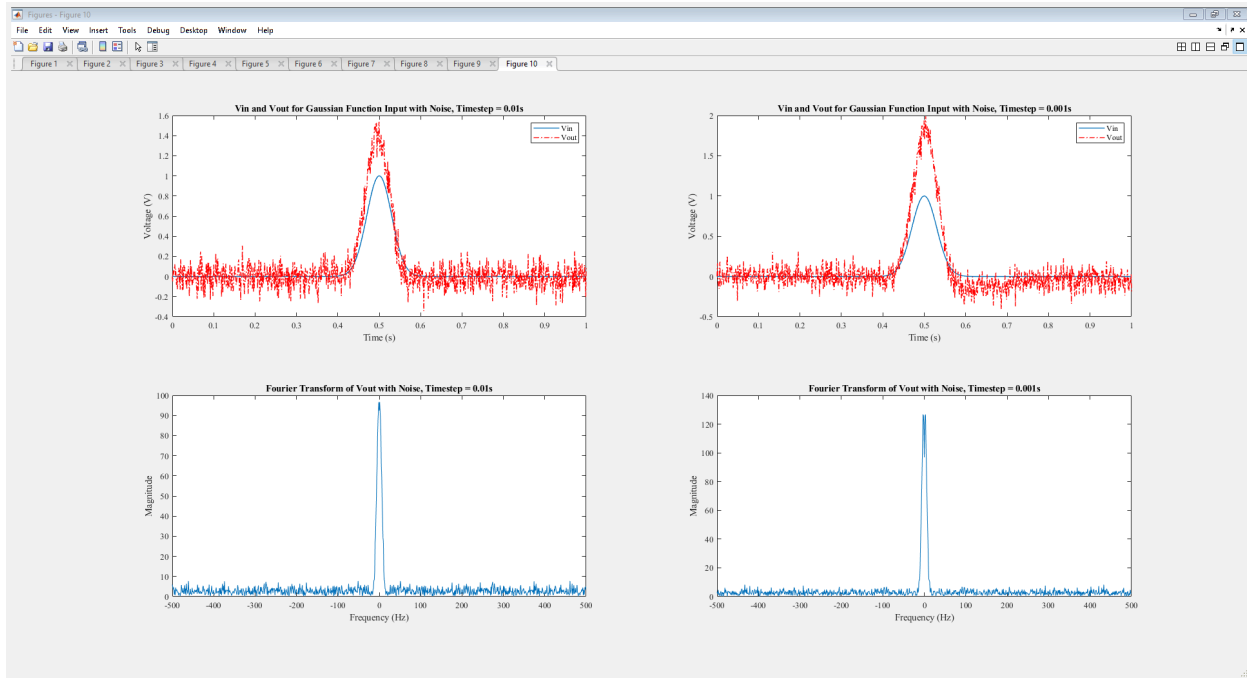

Section 4: Non-Linearity

For a non-linear circuit solution as presented, a new matrix would be required in the time-domain equation to represent the non-linear elements. The modifications to the equation may be represented as $C * (dx/dt) + Gx + H(x) - F(t) = 0$, where $H(x)$ is the new matrix. The purpose of this is to enable the solution via Newton-Raphson iteration, where the non-linear equation and its derivative (Jacobian) can be used to find the solution at the next time step, and the end of the solution can be determined by the reduction of errors in the solution compared to each previous step. To implement this in the circuit, first the DC solution of the circuit would be found using an initial assumption for the DC solution of x , and iterate until a stable solution was found. This solution would then serve as the starting point of the AC analysis, when $t=0$. Then, the problem can be solved using modified Backwards Euler equations or other integration methods.

Published with MATLAB® R2021b